




EE342 Lab-4

Instructions and Example Designs

Mehmet Çalı

2-Line Serial Transmitter/Receiver

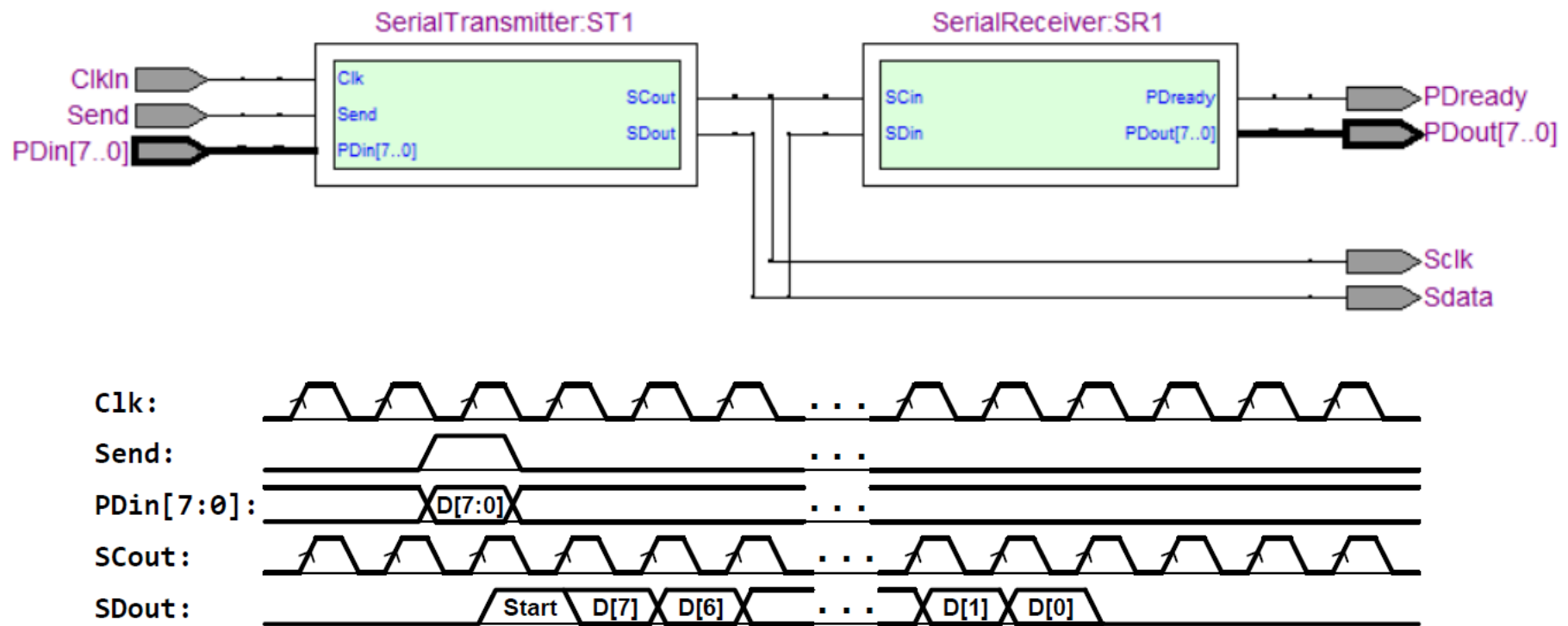- You have seen the 3 line serial transmission in Lecture Notes-5 Serial Interface.
- You are now required to design a 2 line transmitter and receiver and connect them in a top module



Transmitter

- **Inputs:**
 - **Clk:** 20 MHz clock
 - **Send:** 1 Clock cycle signal to inform that the paralel input is ready
 - **Pdata[7:0]** Parallel data
- **Outputs:**
 - **SCLK:** 20 MHz clock
 - **Sdata:** Serial output signal that consist of a start bit and serialized Pdata from MSB to LSB

In three line transmitter we have seen that transmitter consist of a counter and a shift register:

```
// Describe the shift register:
reg [7:0] SR; // 8-bit shift register to store 8-bit parallel data

always @(posedge Clk)
begin
    if (WE == 1'b1)
        SR[7:0] <= Pdata[7:0]; // store parallel input data
    else
        begin // start shifting when WE is 0
            SR[7:1] <= SR[6:0]; // MSB goes out first
            SR[0] <= 1'b0; // clear LSB while shifting left
        end
    end
end
assign Sdata = SR[7]; // MSB of shift register is the Sdata output
```

Transmitter

```
// Describe the counter (a better way):
reg [2:0] Cntr; // 3-bit counter for Sen timing
reg SRshift;    // set while shift register is active

always @(posedge Clk) // a simple counter enabled by SRshift
begin
    if (SRshift == 1'b0)
        Cntr[2:0] <= 3'd0; // reset the counter
    else
        Cntr[2:0] <= Cntr[2:0] + 3'd1; // increment the counter
end


always @(posedge Clk)
begin
    if (WE == 1'b1)
        SRshift <= 1'b1; // set when parallel data is loaded
    else
        if (Cntr[2:0] == 3'd7)
            SRshift <= 1'b0; // reset when counter reaches 7
        else
            SRshift <= SRshift; // keep the last value
end

assign Sen = SRshift; // Sen is free from glitches
```

We do not need this part in our 2 line transmitter however a similar structure will be needed in the receiver part


Receiver

 - **Inputs:**
 - **SCin:** 20 MHz clock
 - **Sdin:** Serial data
- **Outputs:**
 - **PDout[7:0]:** Parallel data
 - **PDready:** One clock cycle signal that indicates the parallel data is ready




Waveform tips

 - You should connect outputs of transmitter and inputs of receiver
- You should create a single waveform file to test your top module with the following nodes



Waveform tips

 - Assign PDin to a asymmetric 8 bit number in unsigned decimal format
- The most and the least significant bits should be one





Arbitrary value

Radix:

Numeric or named value:

Waveform tips

 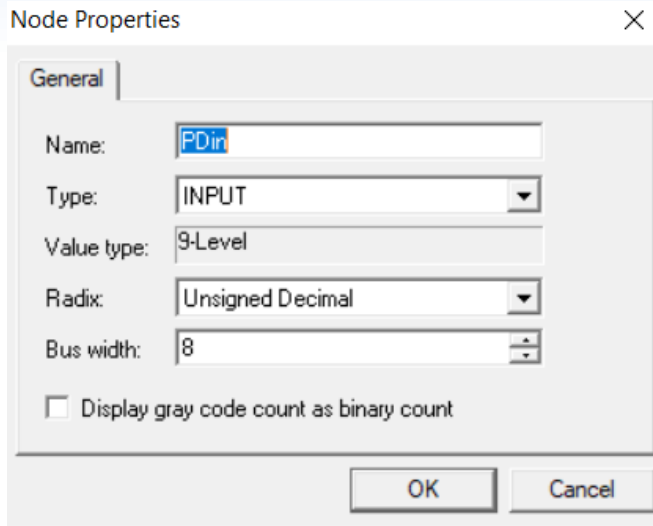- From right click to node name > Properties, assign Radix tab to unsigned decimal for PDin, serial receiver counter and PDout as well




- Be sure that parallel output is same as parallel input and the Pdready signal is set when Pdout is completely received as shown above

Some related design examples

- Before the transmission of signals, they are usually encoded in various ways
- One of the most basic one is differential coding
- In differential coding the signal is encoded according to changes in the encoded output from the original signal

	t1	t2	t3	t4	t5	t6	t7	t8
Original signal x(i)	1	0	1	0	0	0	1	0
Encoded signal y(i)	0	1	0	0	0	0	1	1



$$y(i) = y(i - 1) \wedge x(i)$$

 

Differential Coding

- Wrong approach-1:
 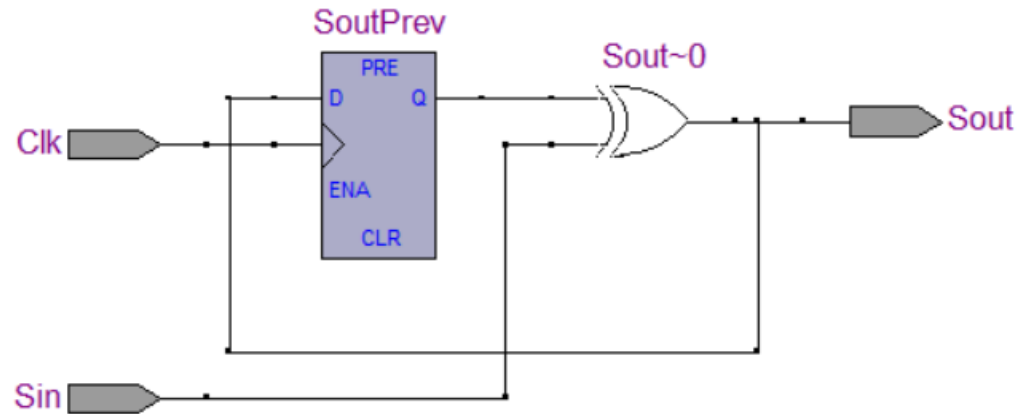
```
1  `ifdef part1
2      //Differential encoding
3  module example1(Sin, Clk, Sout)
4      input Sin, Clk;
5      output Sout;
6      reg SoutPrev;
7
8      always @(posedge Clk)
9      begin
10         SoutPrev = Sout;
11     end
12
13     assign Sout = SoutPrev ^ Sin;
14
15 endmodule
16
17
18 `endif
```



Differential Coding

- Wrong approach-2:

```
`ifndef part1a


    //Differential encoding
    module example1(Sin, Clk, Sout);
    input Sin, Clk;
    output reg Sout;
    reg SoutPrev;

    always @(posedge Clk)
    begin
        SoutPrev <= Sout;
    end

    always @(posedge Clk)
    begin
        Sout <= SoutPrev ^ Sin;
    end


    endmodule

`endif
```

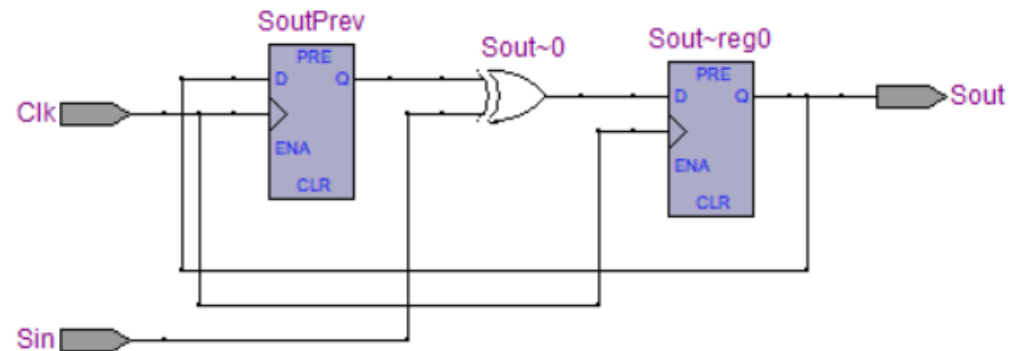

Differential Coding


Result of wrong approach-2:

 


Third approach:

```
`ifdef part1b
//Differential encoding
module example1(Sin, Clk, Sout);
input Sin, Clk;
output reg Sout;

 always @(posedge Clk)
begin
    Sout <= Sout ^ Sin;
end
endmodule
`endif
```




Result of third approach:

 

Differential Coding


- After the optional encoding process serialized signal can be sent in various line number.
- You have seen the three line transmission and you are responsible for the two line transmission in the next week. What about single line transmission?
- Single line transmission obviously involves transmission of the data without a clock signal
- When we lower the line number from 3 to 2 by removing the data enable signal, we could extract it from the start bit in the receiver side.
- How could we extract the clock signal at the receiver side?
- There are various ways, but we will start with a first phase of a relatively simple clock extractor approach

 

Edge Detection

- In order to extract the clock signal with a proper phase from the data, we need a high frequency input clock with arbitrary phase and a edge detection circuit in the method that we will apply.
- Edge detection will be applied to the data so that we could generate a clock from higher frequency clock whose rising clock edge will correspond to the middle section of the data

Edge detector reference schematic:

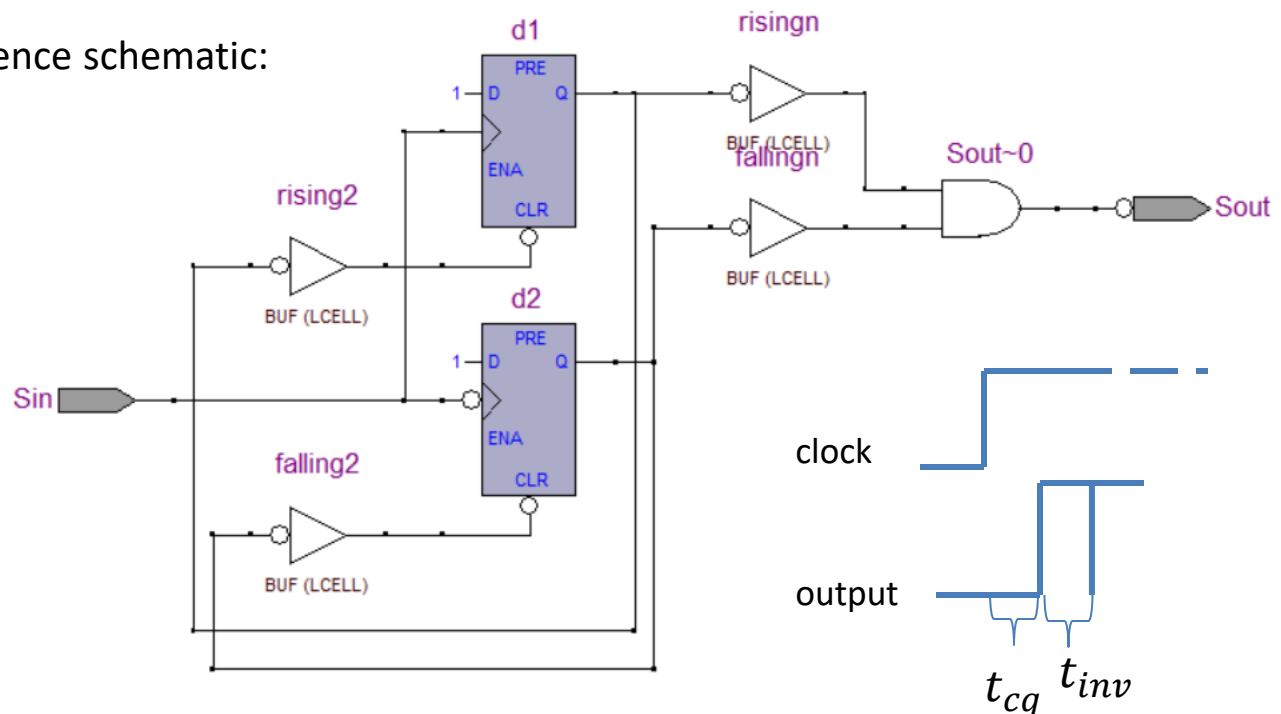

Edge Detection

```

`ifdef part3
module example1(Sin, Sout);
input Sin;
output Sout;
wire rising, falling;

supply1 vcc;
supply0 gnd;


DFF d1
(
    .d(vcc),
    .clk(Sin),
    .clrn(~rising),
    .prn(vcc),
    .q(rising)
);

DFF d2
(
    .d(vcc),
    .clk(~Sin),
    .clrn(~falling),
    .prn(vcc),
    .q(falling)
);


assign Sout = rising || falling;
endmodule
`endif

```

- Edge detector reference output:

 


- Edge detector reference schematic:

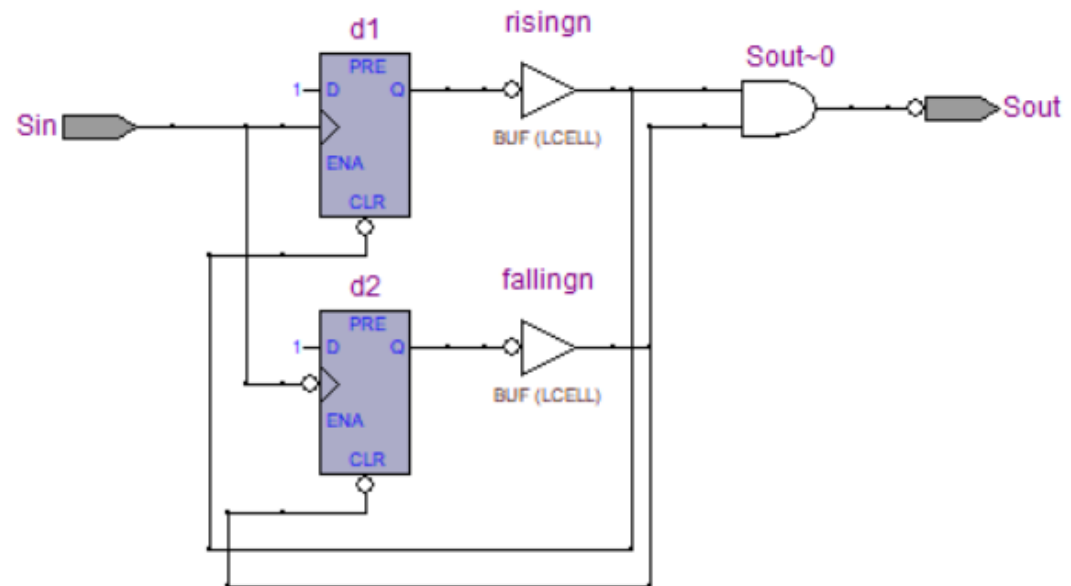

Edge Detection

- Part-3 schematic:

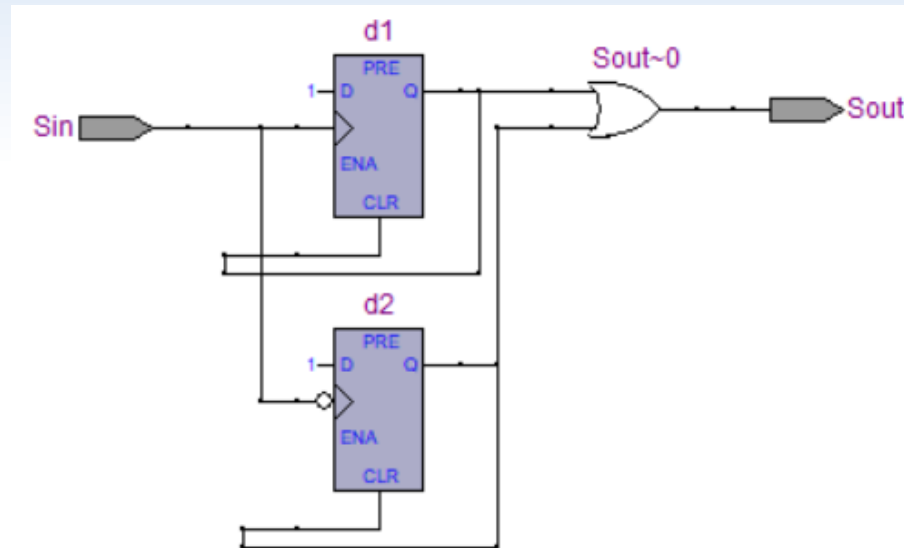

- Part-3 waveform:

